

$$V_T = 25 \text{ mV}$$

$$\beta = 255$$


QUESTION 1

10 points

Save Answer

For the emitter follower circuit (EF) shown below, find the value for the input impedance R_{in} in ($M\Omega$) if current $I_C = 1.4 \text{ mA}$, given that $R_E = 10 \text{ k}\Omega$, $R_S = 0$, $R_L = \infty$.

$$R_{in} = \frac{V_T}{I_C} + (\beta + 1) \cdot R_E$$

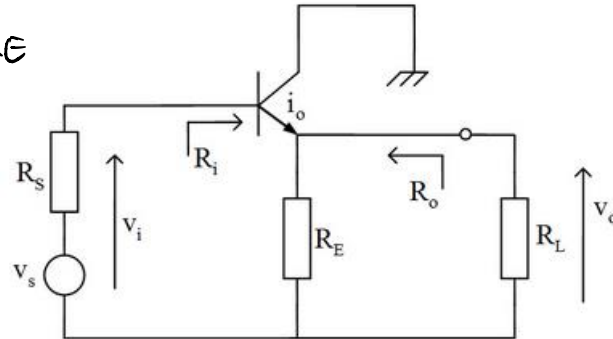

QUESTION 2

10 points


Save Answer

For the Widlar current mirror circuit shown below, design the circuit to provide a current $I_{out} = 100 \mu\text{A}$, if $I_{R2} = 612 \mu\text{A}$. Hence, find the value of R_2 (in $k\Omega$).

KVL

$$9V - V_{EB} - R_2 I_{R2} = 0$$

$$\frac{9V - V_{EB}}{I_{R2}} = R_2$$

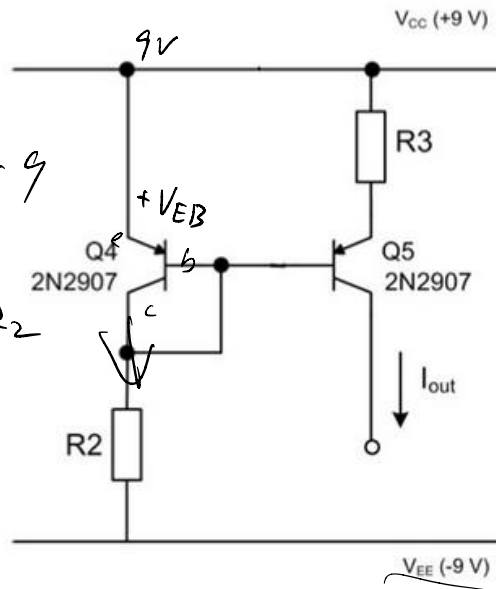


$$I_o R_E = \ln \left(\frac{I_{ref}}{I_o} \right)$$

QUESTION 3

10 points

Save Answer

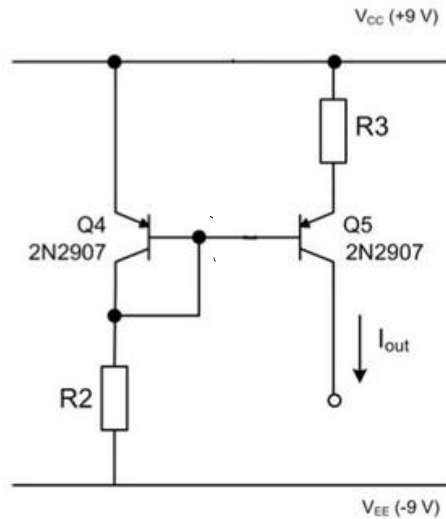For the Widlar current mirror circuit shown below, design the circuit to provide a current $I_{out}=100\mu A$, if $I_{R2}=685\mu A$. Hence, find the value of R_3 (in Ω), given that $V_T=25mV$.



$$= 250 \ln \left(\frac{I_{R2}}{I_{out}} \right)$$


QUESTION 4

5 points

Save Answer

For the simple current mirror circuit shown below, find the value of R_2 in ($k\Omega$) to provide the current $I_{out}=3mA$.

$$R_2 = \frac{17.4}{I_{out}}$$

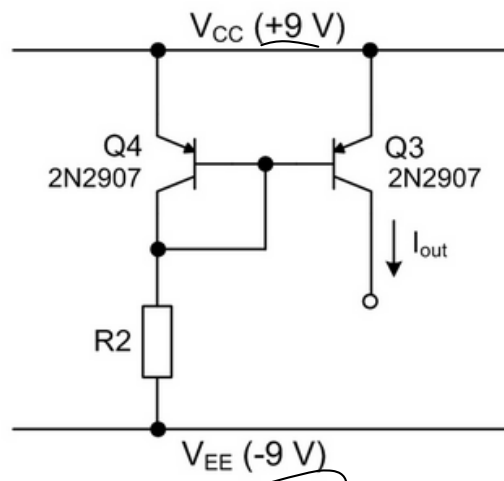

QUESTION 5


10 points

Save Answer

For the emitter follower circuit (EF) shown below, find the value for the output impedance R_{out} in (Ω) if current $I_C=7.8\text{mA}$, given that $R_E=10\text{k}\Omega$, $R_S=0$, $R_L=\infty$.

$$g_m = \frac{I_C}{V_T} \quad r_b = \frac{\beta}{g_m}$$

$$R_o = \frac{1}{\frac{1}{r_b} + \frac{1}{R_E} + g_m}$$

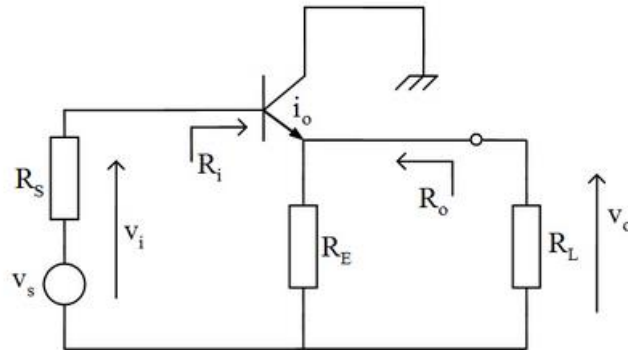


QUESTION 6

10 points

Save Answer

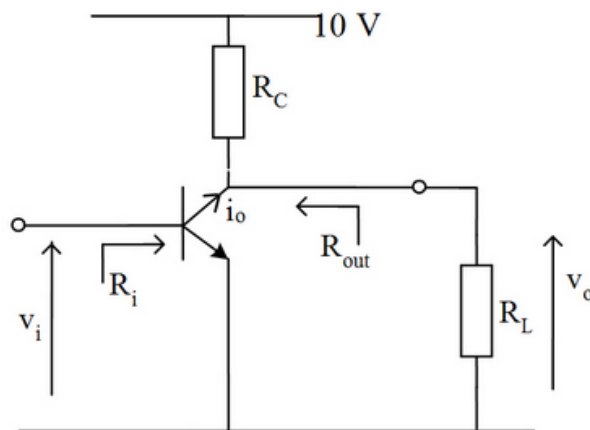For the common emitter (CE) circuit shown below, find the value for the output impedance R_{out} in ($\text{k}\Omega$) if current $I_C=4\text{mA}$, given that $R_C=10\text{k}\Omega$, $V_A=150\text{V}$, $R_L=\infty$.



$$r_o = \frac{V_A}{I_C}$$

$$R_{out} = r_o \parallel R_C =$$

QUESTION 7


10 points

Save Answer

For the common emitter circuit (CE) shown below, find the value for the voltage gain A_V if the current $I_C = 4.6 \text{ mA}$, given that $R_C = 10 \text{ k}\Omega$, $V_A = 150 \text{ V}$, $R_L = \infty$.

$$g_m = \frac{I_C}{V_T} \quad r_o = \frac{V_A}{I_C}$$

$$A_V = -g_m (R_C \parallel r_o)$$

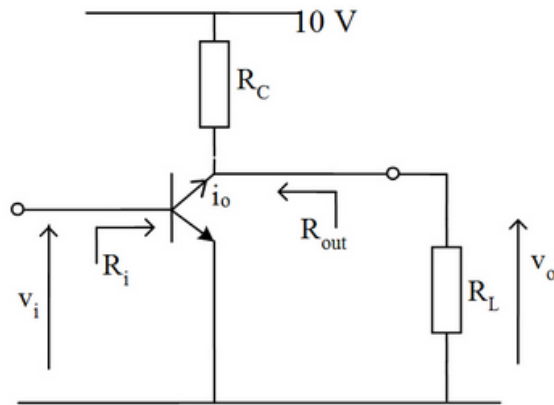


QUESTION 8

5 points

Save Answer

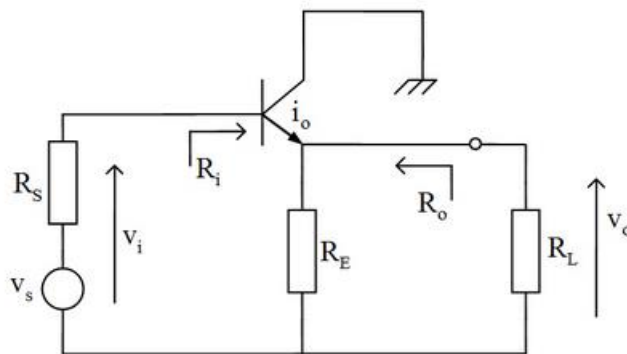For the emitter follower circuit (EF) shown below, find the value for voltage gain (A_V) if current $I_C = 2.7 \text{ mA}$, given that $R_E = 10 \text{ k}\Omega$, $R_S = 0$, $R_L = \infty$.



$$I_C \approx I_E = 2.7 \text{ mA}$$

$$V_o = I_E R_E$$

$$-V_i + 0.6 + I_E R_E = 0$$

$$\therefore V_i = 0.6 + I_E R_E$$

$$= 0.6 + 27$$

$$A_V = \frac{V_o}{V_i} = \frac{27}{27.6}$$


QUESTION 9

5 points

Save Answer

For the differential input stage shown below, the differential input impedance is required to be $100\text{k}\Omega$. Estimate the bias current in the differential amplifier to meet this specification. Hence calculate the value of R_2 (in $\text{k}\Omega$) required to set this bias current. The Early voltage of the NPN transistor is 150 V and that for the PNP is 50 V .

68.2

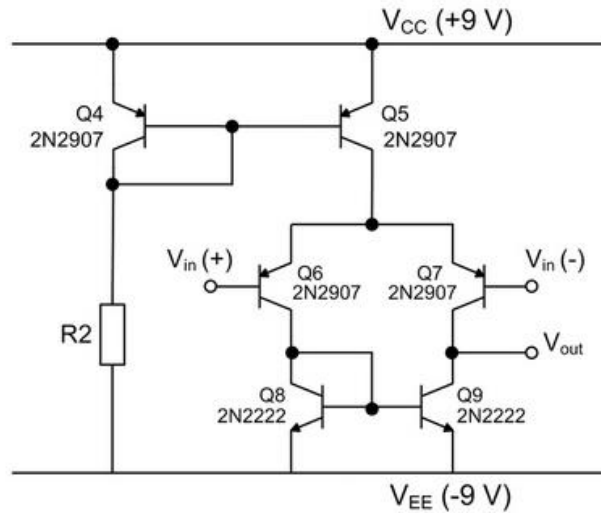

QUESTION 10


10 points

Save Answer

For the differential input stage shown below, the differential input impedance is required to be $100\text{k}\Omega$. Estimate the bias current in the differential amplifier to meet this specification. Hence calculate the value of the differential gain A_{vD} . The Early voltage of the NPN transistor is 150 V and that for the PNP is 50 V .

1500.001

$$r_e = \frac{V_T}{(\beta + 1) I_B}$$

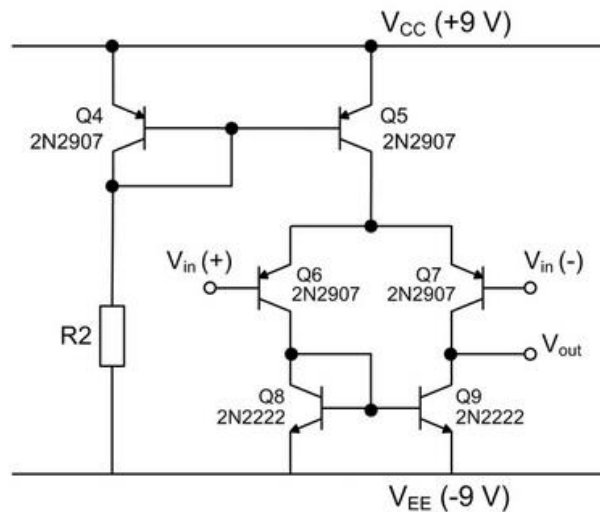


QUESTION 11

5 points

Save Answer

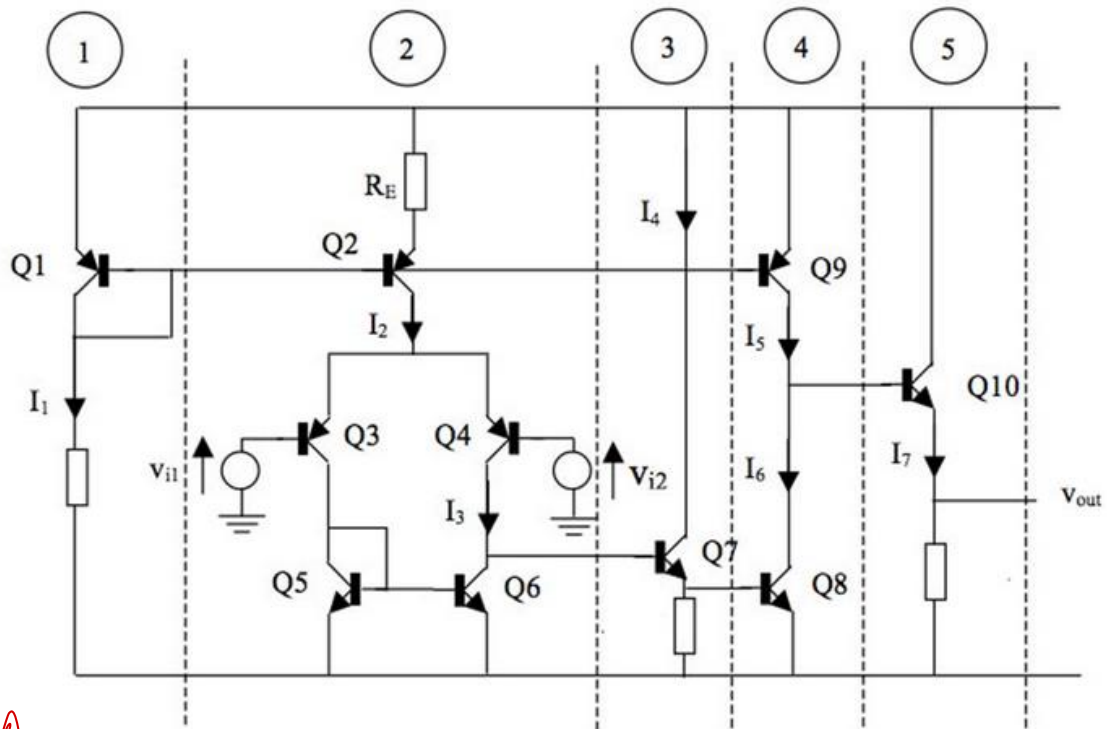Match each of the stages shown in the circuit below with its purpose:



- ☒ Stage 1
- ☒ Stage 2/4
- ☒ Stage 3
- ☒ Stage 5

- A. set the DC bias for all stages
- B. 'match' the gain stages to avoid loading effects
- C. provide high voltage gain
- D. provide low output resistance

QUESTION 12

5 points

Save Answer

The emitter follower amplifier (EF) has input impedance, output impedance and voltage gain. (Hint: use 'high' and 'low' to fill in the blanks)

QUESTION 13

5 points

Save Answer

The common emitter amplifier (CE) has output impedance and voltage gain. (Hint: use 'high' and 'low' to fill in the blanks)