

# Op-amp Design (expt.5)

- **Design** and simulate in Multisim, an operational amplifier circuit.
- The four 'building blocks' are:
  - differential input stage (long-tailed pair)
  - common emitter amplifier
  - emitter follower
  - current mirror circuit
- Briefly investigate each of these circuits in turn before combining them to produce the operational amplifier circuit to a given specification.


These slides are on CANVAS under 'Experiment 5'

# Specification

- Differential input impedance,  $R_{id} > 100 \text{ k}\Omega$
- Voltage gain ( $A_{ol}$ ) greater than 500,000
- Output impedance,  $R_o < 1 \text{ k}\Omega$
- Output voltage to be 'zero' volts for zero input
- Frequency response down to D.C.
- Supply voltage +9 to -9 V
- total current consumption not greater than 5 mA

# DC characteristics

[see 'Part 2' slides on CANVAS]

 

Common-emitter, **DC**  
current gain

$$h_{FE} = \frac{I_C}{I_B}$$


Common-emitter, **AC**  
current gain

$$h_{fe} = \frac{\Delta I_C}{\Delta I_B} = \frac{i_c}{i_b}$$

Q: How could we estimate AC gain from DC characteristics?


Note: different notation
 
$$h_{FE} \equiv \beta \quad h_{fe} \equiv \beta_o$$




 
# Pre-lab


- Learn how to design the 'building blocks'




Part 2 Notes  
EF and CE  
stages

  

Part 4 Notes  
Simple CM

 


Part 4 Notes  
Widlar CM

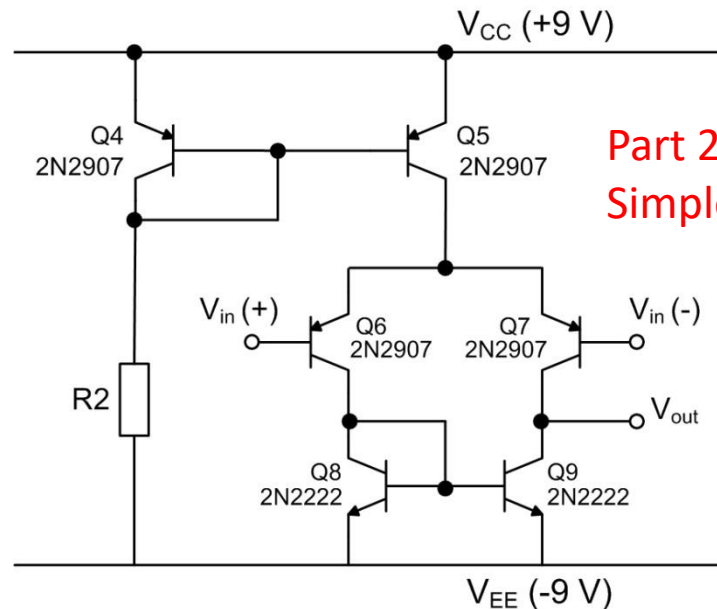


Part 2 Notes  
Simple CM

Part 3 notes  
Differential Amp  
Part 5 Notes  
Active loads



# Putting it together...

 

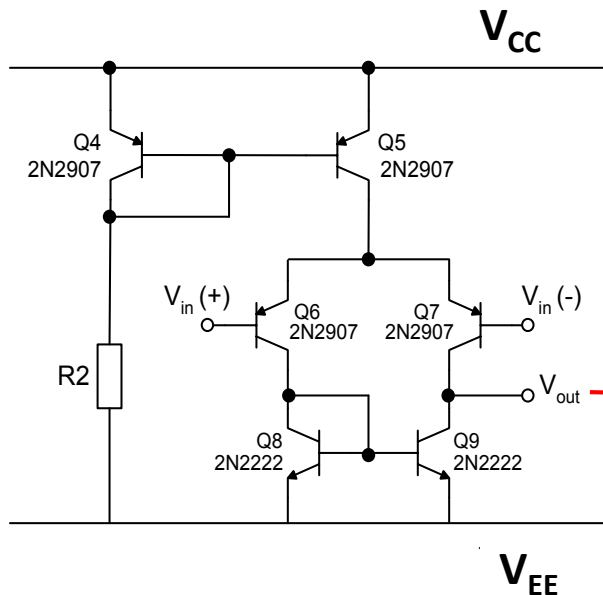May need another block to meet the spec on  $R_{OUT}...$



  
A CC stage to match the input and **CE** voltage gain stages



Use an active load here, not a resistor or you won't get enough gain

- Always check the dc levels (voltages, currents) first
- Remember loading effects of one stage on another


# CE amp with CM load

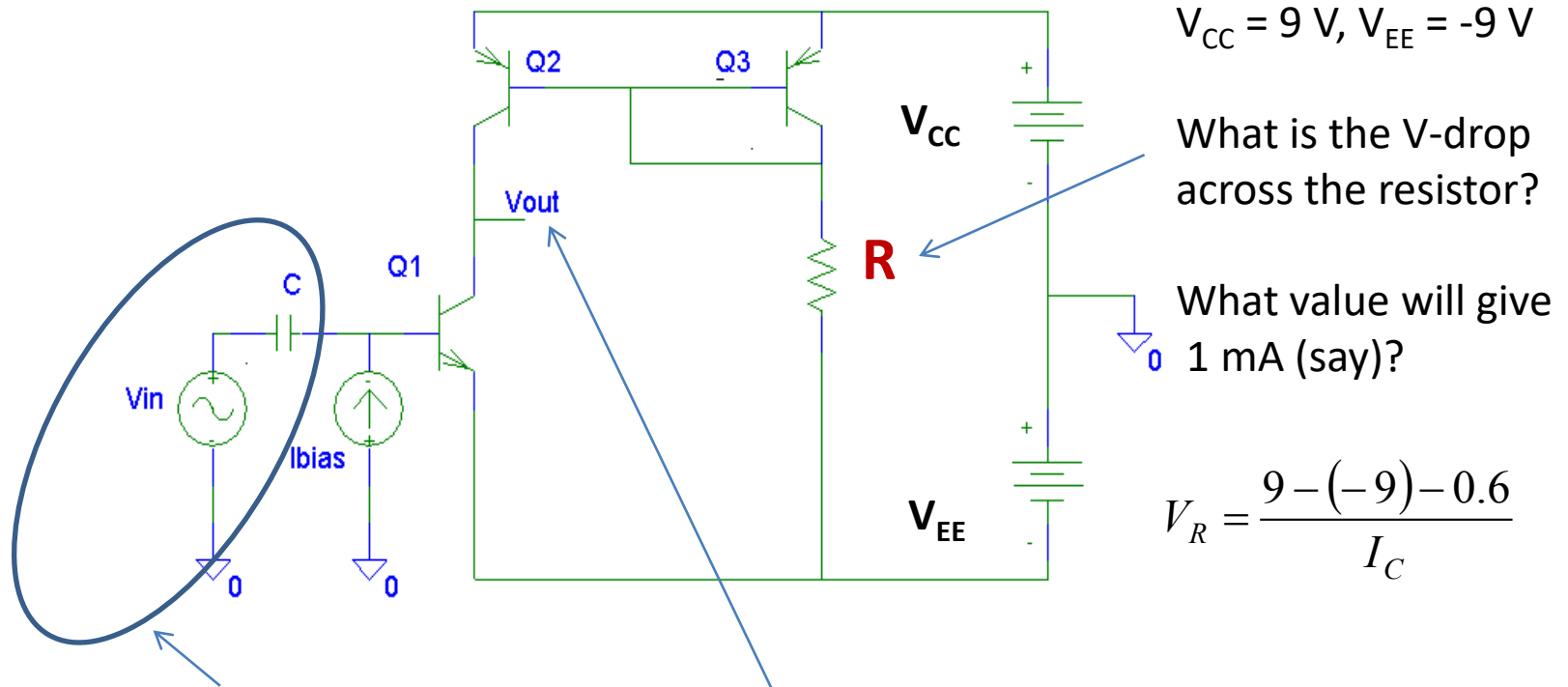

Can use this to check the gain once you have it biased correctly

Set  $I_C$  to your desired value  
Choose  $I_{bias}$  to set  $V_{out} \approx 0\text{ V}$   
(use a dc sweep of  $I_{bias}$  as before)
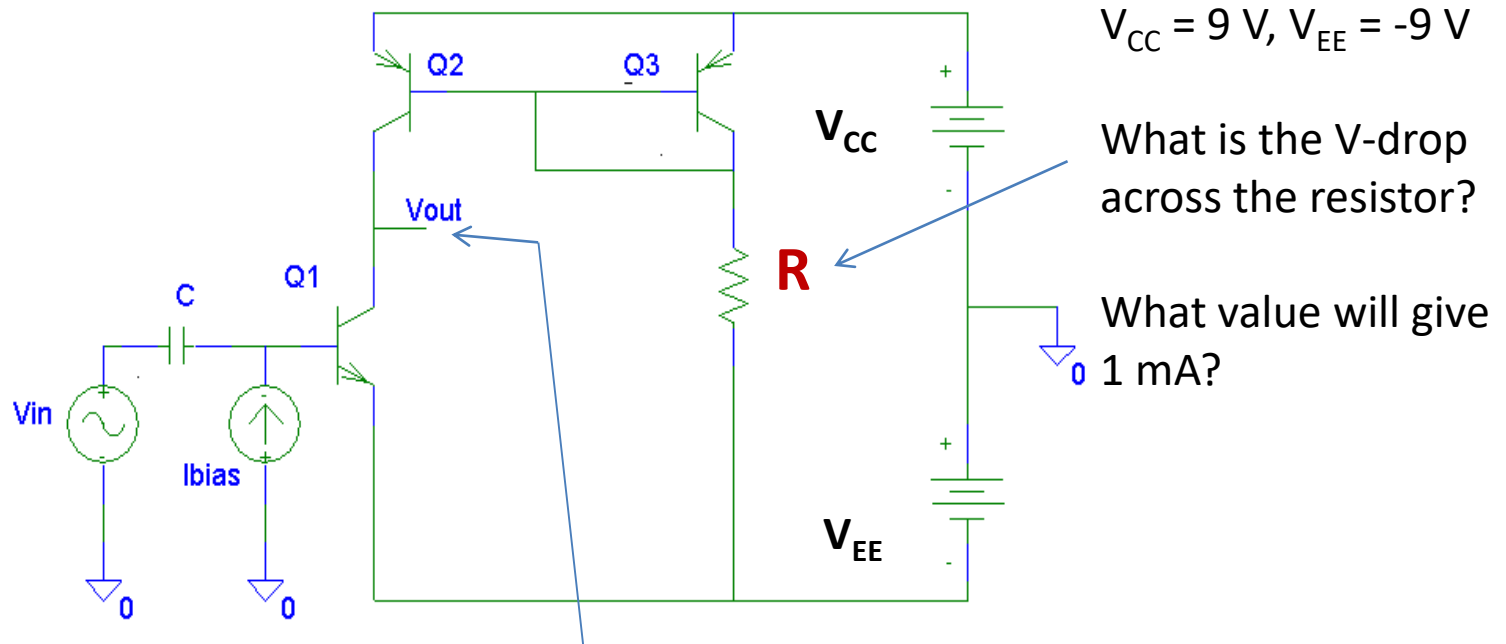
# Output resistance of a CE amp with CM load



$$r_{ce} = \frac{V_A}{I_C}$$

$$R_{OUT} = r_{ce1} \parallel r_{ce2}$$


You can find the Early voltage from the model listing for the transistor

If the CE is connected to a load (another stage), it's ac load is

$$r_{ce1} \parallel r_{ce2} \parallel R_{in}(\text{next stage})$$

Same analysis applies for the Diff Amp output

# Matching the Diff Amp to the CE

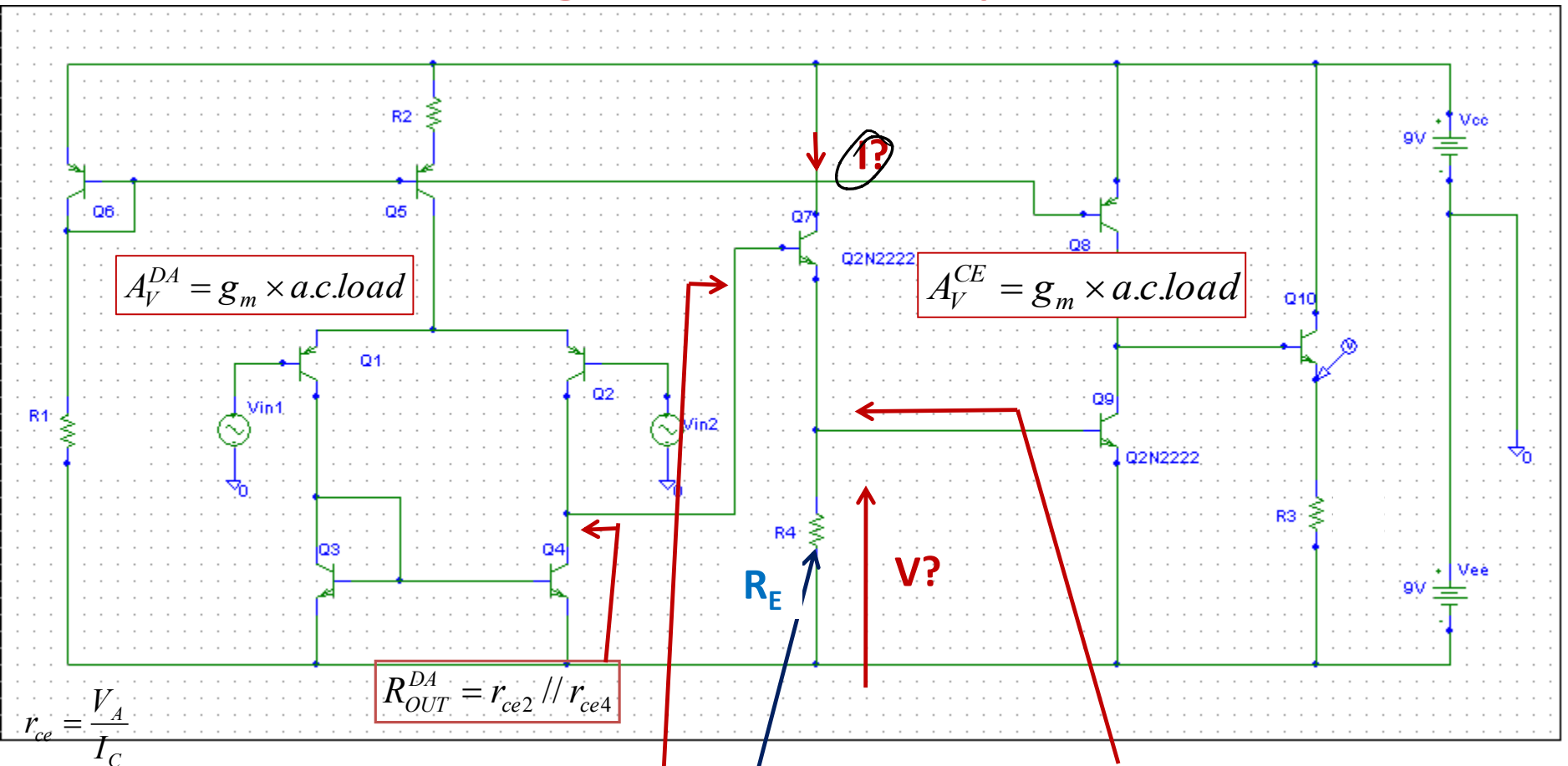

$R_E$  effectively acts as a current source (with  $V_{EE}$ )


$$r_{be} = \frac{\beta_o}{g_m} = \frac{\beta_o}{40I}$$

Ac load for Diff. amp. is  $r_{ce2} \parallel r_{ce4} \parallel R_{in}(CC)$



 
# The VTC is a handy way to estimate gain (and investigate offsets)

First, look at the **Voltage Transfer Curve** (VTC) of an amplifier.



Sweep the voltage on the positive input


Attach the negative input to ground)

 

Usually see a small voltage offset here:  
Measure it and then build into the input  
voltage source to set the output close to 0 V.
 
# Or: alternative way to measure $A_{ol}$

- Measuring the very high  $A_{ol}$  is problematic as the amplifier is unstable.
- A method for measuring  $A_{ol}$  is shown below.



$$A_{ol} = \frac{v_o}{v_Y} \times 101$$

**Exercise:** Prove the equation by equating currents between  $v_Y$  and ground

# Hints for calculations

## Design Notes Expt 5

Setting the differential input resistance

$$R_{id} = 2r_{be} = \frac{2\beta_o}{g_m} = \frac{2\beta_o}{40I_C}$$

So bias current,  $I_O$  in differential amplifier is

$$I_O = 2I_C = 2 \frac{2\beta_o}{40R_{id}}$$

$$I_O = \frac{\beta_o}{10R_{id}}$$

Now to design the Widlar current mirror to bias the diff amp stage.

$$R_E I_O = V_T \ln \left( \frac{I_{ref}}{I_O} \right) \text{ or } I_{ref} = I_O \exp \left( \frac{I_O R_E}{V_T} \right)$$

Don't know  $R_E$  or  $I_{ref}$

Try  $I_O R_E = V_T$

# Some advice

- Study the script and think about the design beforehand..
- **Use your ELEC271 notes!**
- **Bring your record of the pre-lab questions to the laboratory – needed when designing the complete OPAMP circuit.**
- Always check dc levels FIRST!! – check they are as expected
- Remember loading effects of one stage on another (Part 2 notes)
- Ask questions
- Good luck